

Use this diagram to help you create a circuit with a switch.
You can record observations or ideas below.

