

Use this diagram to help you create a parallel circuit.  
You can record observations or ideas below.

