

Use this diagram to help you create a simple circuit.  
You can record observations or ideas below.

